

Series and Parallel Circuit Analysis

- 1) How would the brightness of the individual bulbs in a series circuit change as bulbs of the same resistance are added?

- reduce brightness
 ↳ series circuit, brightness controlled by V

- 2) If one bulb (1 ohm) is in a series circuit and the switch is open what is the voltage drop across the lamp?

Zero
 ↳ switch is open

- 3) What happens to the amount of current in a series circuit when two more 1 Ω resistors are added to it?

$V = IR$ - voltage is the same, but R is increased
 $I = \frac{V}{R}$ ∴ current decreases


- 4) Solve the following circuits.



	V	I	R
R_1	30	0.3A	100
Total	30	0.3A	100

$$I = \frac{V}{R} = 0.3A$$

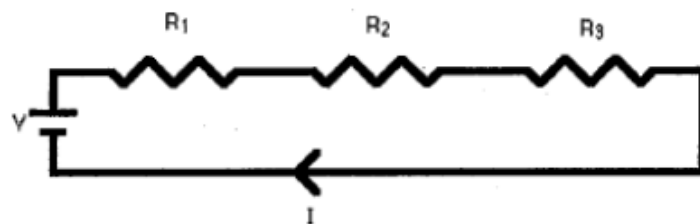$R_1 = 8 \Omega$, $R_2 = 8 \Omega$, and $R_3 = 4 \Omega$. The cell is a 10 V cell.




	V	I	R
R_1	4 V	0.5A	8 Ω
R_2	4 V	0.5A	8 Ω
R_3	2 V	0.5A	4 Ω
Total	10 V	0.5A	20 Ω

$$I = \frac{V}{R}$$


$$I = \frac{10V}{20\Omega}$$

$$I = 0.5A$$

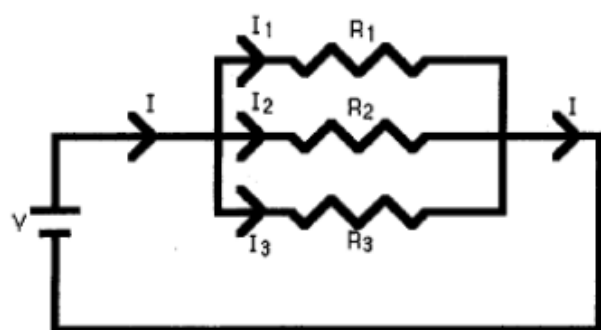


	V	I	R
R ₁	10V	1.25A	8Ω
R ₂	10V	1.25A	8Ω
R ₃	10V	2.5A	4Ω
Total	10V	5A	2Ω
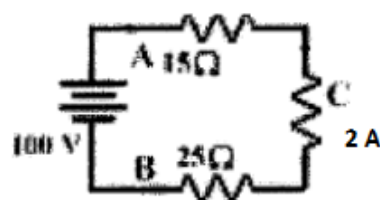
$$\frac{1}{R_T} = \frac{1}{8\Omega} + \frac{1}{8\Omega} + \frac{1}{4\Omega} = \frac{1}{2\Omega} \Rightarrow R_T = 2\Omega$$




	V	I	R
R _A	30V	2A	15Ω
R _B	50V	2A	25Ω
R _C	20V	2A	10Ω
Total	100V	2A	50Ω

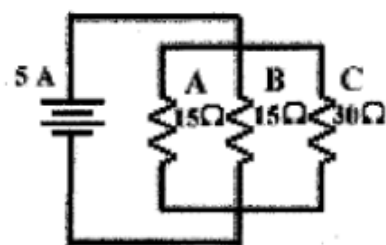

	V	I	R
R _A	30V	2A	15Ω
R _B	30V	2A	15Ω
R _C	30V	1A	30Ω
Total	30V	5A	6Ω
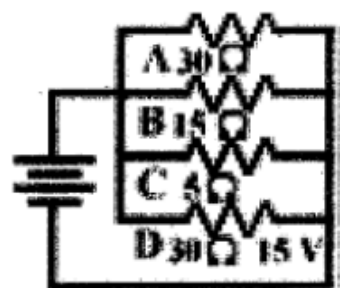
$$\frac{1}{R_T} = \frac{1}{15\Omega} + \frac{1}{15\Omega} + \frac{1}{30\Omega}$$



	V	I	R
R _A	15V	0.5A	30Ω
R _B	15V	1A	15Ω
R _C	15V	3A	5Ω
Total R _D	15V	0.5A	30Ω
Total	15V	5A	3Ω

$$\frac{1}{R_T} = \frac{1}{30} + \frac{1}{15} + \frac{1}{5} + \frac{1}{30}$$

- 5) How would the brightness of the individual bulbs in a parallel circuit change as bulbs of the same resistance are added?

- does not change as long as the power source can provide the same I